

Department of Electrical and Computer Engineering

Author: Zainab Hussein

Title: Multicycle Processor (Part 1)

Date: 4-11-2017

1. Time spent: Lab period
2. Table 4

State (Name)	PCWrite	MemWrite	IRWrite	RegWrite	ALUSrcA	Branch	Iord	MemtoReg	RegDst	ALUSrcB[1:0]	PCSrc[1:0]	ALUOp[1:0]	FSM Control Word
0 (Fetch)	1	0	1	0	0	0	0	0	0	01	00	00	0x5010
1 (Decode)	0	0	0	0	0	0	0	0	0	11	00	00	0x0030
2 (MemAdr)	0	0	0	0	1	0	0	0	0	10	00	00	0x0420
3 (MemRd)	0	0	0	0	0	0	1	0	0	00	00	00	0x0100
4 (MemWB)	0	0	0	1	0	0	0	1	0	00	00	00	0x0880
5 (MemWr)	0	1	0	0	0	0	1	0	0	00	00	00	0x2100
6 (RtypeEx)	0	0	0	0	1	0	0	0	0	00	00	10	0x0402
7 (RtypeWB)	0	0	0	1	0	0	0	0	1	00	00	00	0x0840
8 (BeqEx)	0	0	0	0	1	1	0	0	0	00	01	01	0x0605
9 (AddiEx)	0	0	0	0	1	0	0	0	0	10	00	00	0x0420
10 (AddiWB)	0	0	0	1	0	0	0	0	0	00	00	00	0x0800
11 (JEx)	1	0	0	0	0	0	0	0	0	00	10	00	0x4008

3. Controller, maindec and aludec code

```

module controller(input logic      clk, reset,
                  input logic [5:0] op, funct,
                  input logic      zero,
                  output logic      pcen, memwrite, irwrite, regwrite,
                  output logic      alusrcA, iord, memtoReg, regdst,
                  output logic [1:0] alusrcB, pcsrc,
                  output logic [2:0] alucontrol);

logic [1:0] aluop;
logic      branch, pcwrite;

```

```

assign pcen = pcwrite|(branch&zero);
// Main Decoder and ALU Decoder subunits.
maindec md(clk, reset, op,
           pcwrite, memwrite, irwrite, regwrite,
           alusrca, branch, iord, memtoreg, regdst,
           alusrcb, pcsrc, aluop);
aludec ad(funct, aluop, alucontrol);
// ADD CODE HERE
// Add combinational logic (i.e. an assign statement)
// to produce the PCEn signal (pcen) from the branch,
// zero, and pcwrite signals
endmodule

module maindec(input  logic      clk, reset,
               input  logic [5:0] op,
               output logic      pcwrite, memwrite, irwrite, regwrite,
               output logic      alusrca, branch, iord, memtoreg, regdst,
               output logic [1:0] alusrcb, pcsrc,
               output logic [1:0] aluop);

parameter FETCH  = 4'b0000;    // State 0
parameter DECODE = 4'b0001;    // State 1
parameter MEMADR = 4'b0010;    // State 2
parameter MEMRD  = 4'b0011;    // State 3
parameter MEMWB  = 4'b0100;    // State 4
parameter MEMWR  = 4'b0101;    // State 5
parameter RTYPEEX = 4'b0110;   // State 6
parameter RTYPEWB = 4'b0111;   // State 7
parameter BEQEX   = 4'b1000;   // State 8
parameter ADDIEX  = 4'b1001;   // State 9
parameter ADDIWB  = 4'b1010;   // state 10
parameter JEX     = 4'b1011;   // State 11
parameter LW      = 6'b100011; // Opcode for lw
parameter SW      = 6'b101011; // Opcode for sw
parameter RTYPE   = 6'b000000; // Opcode for R-type

```

```

parameter  BEQ      = 6'b000100;    // Opcode for beq
parameter  ADDI     = 6'b001000;    // Opcode for addi
parameter  J        = 6'b000010;    // Opcode for j
logic [3:0] state, nextstate;
logic [14:0] controls;
// state register
always_ff @(posedge clk or posedge reset)
    if(reset) state <= FETCH;
    else state <= nextstate;
// ADD CODE HERE
// Finish entering the next state logic below.  We've completed the first
// two states, FETCH and DECODE, for you.
// next state logic
always_comb
    case(state)
        FETCH:  nextstate <= DECODE;
        DECODE: case(op)
            LW:      nextstate <= MEMADR;
            SW:      nextstate <= MEMADR;
            RTYPE:   nextstate <= RTYPEEX;
            BEQ:     nextstate <= BEQEX;
            ADDI:    nextstate <= ADDIEX;
            J:       nextstate <= JEX;
            default: nextstate <= 4'bx; // should never happen
        endcase
        // Add code here
        MEMADR: case(op)
            LW:      nextstate <= MEMRD;
            SW:      nextstate <= MEMWR;
            default: nextstate <= 4'bx; // should never happen
        endcase
        MEMRD:  nextstate <= MEMWB;
        MEMWB:  nextstate <= FETCH;
        MEMWR:  nextstate <= FETCH;
    endcase

```

```

    RTYPEEX: nextstate <= RTYPEWB;
    RTYPEWB: nextstate <= FETCH;
    BEQEX:   nextstate <= FETCH;
    ADDIEX:  nextstate <= ADDIWB;
    ADDIWB:  nextstate <= FETCH;
    JEX:     nextstate <= FETCH;

    default: nextstate <= 4'bx; // should never happen
endcase

// output logic
assign {pcwrite, memwrite, irwrite, regwrite,
        alusrca, branch, iord, memtoreg, regdst,
        alusrcb, pcsrc, aluop} = controls;

// ADD CODE HERE

// Finish entering the output logic below. We've entered the
// output logic for the first two states, S0 and S1, for you.
always_comb
    case(state)
        FETCH: controls <= 15'h5010;
        DECODE: controls <= 15'h0030;

        // your code goes here

        MEMADR: controls <= 15'h0420;
        MEMRD:  controls <= 15'h0100;
        MEMWB:  controls <= 15'h0880;
        MEMWR:  controls <= 15'h2100;
        RTYPEEX: controls <= 15'h0402;
        RTYPEWB: controls <= 15'h0840;
        BEQEX:  controls <= 15'h0605;
        ADDIEX: controls <= 15'h0420;
        ADDIWB: controls <= 15'h0800;
        JEX:    controls <= 15'h4008;

        default: controls <= 15'hxxxx; // should never happen
    endcase
endmodule

module aludec(input logic [5:0] funct,

```

```

        input  logic [1:0] aluop,
        output logic [2:0] alucontrol);
// ADD CODE HERE
// Complete the design for the ALU Decoder.
// Your design goes here. Remember that this is a combinational
// module.
// Remember that you may also reuse any code from previous labs.
// beq, addi, j
always_comb
    case(aluop)
        2'b00: alucontrol <= 3'b010; // add, lw, sw
        2'b10: alucontrol <= 3'b110; // sub
        2'b01: alucontrol <= 3'b110; // beq
        2'b11: alucontrol <= 3'b001; // ori //ADDED ORI CONTROL SIGNAL
        default: case(funcnt) // RTYPE
            6'b100000: alucontrol <= 3'b010; // ADD
            6'b100010: alucontrol <= 3'b110; // SUB
            6'b100100: alucontrol <= 3'b000; // AND
            6'b100101: alucontrol <= 3'b001; // OR
            6'b101010: alucontrol <= 3'b111; // SLT
            default: alucontrol <= 3'bxxx; // ???
        endcase
    endcase
endmodule

```

4. Controllertest testbench

```

module controllertest();
    //inputs
    logic      clk, reset;
    logic [5:0] op, funct;
    logic      zero;
    //outputs
    logic      pcen, memwrite, irwrite, regwrite;
    logic      alusrca, iord, memtoreg, regdst;

```

```

logic [1:0] alusrcb, pcsrc;
logic [2:0] alucontrol;

// instantiate device to be tested
controller dut(clk, reset, op, funct, zero,
               pcen, memwrite, irwrite, regwrite,
               alusrcb, iord, memtoreg, regdst,
               alusrcb, pcsrc, alucontrol);

// generate clock to sequence tests
always
    begin
        clk <= 1; # 5; clk <= 0; # 5;
    end

// initialize test
initial begin
    reset= 1 ;
    op= 6 'b000000;
    zero =0 ;
    funct= 6 'b000000;
    //lw test
    @(posedge clk)#40;
    begin
        reset= 0 ;
        op = 6 'b100011;
        zero= 0 ;
        funct= 6 'b000000;
    end
    //sw test
    @(posedge clk)#40;
    begin
        reset= 0 ;
        op = 6 'b101011;
        zero= 0 ;
        funct= 6 'b000000;
    end
end

```

```

end

//add test
@(posedge clk)#40;
begin
    reset= 0 ;
    op = 6 'b000000;
    zero= 0 ;
    funct= 6 'b100000;
end

//sub test
@(posedge clk)#40;
begin
    reset= 0 ;
    op = 6 'b000000;
    zero= 0 ;
    funct= 6 'b100010;
end

//or test
@ (posedge clk)#40;
begin
    reset =0 ;
    op= 6 'b000000;
    zero= 0 ;
    funct =6 'b100101;
end

//slt test
@(posedge clk)#40;
begin
    reset =0 ;
    op= 6 'b000000;
    zero= 0 ;
    funct =6 'b101010;
end


```

```

    //beq test
    @(posedge clk)#40;
    begin
        reset= 0 ;
        op = 6 'b000100;
        zero= 1 ;
        funct= 6 'b000000;
    end
    //addi test
    @(posedge clk)#40;
    begin
        reset= 0 ;
        op = 6 'b001000;
        zero= 0 ;
        funct= 6 'b000000;
    end
    //j test
    @(posedge clk)#40;
    begin
        reset= 0 ;
        op = 6 'b000010;
        zero= 0 ;
        funct= 6 'b000000;
    end
end
endmodule

```



5. Simulation waveforms

  

Expected:

lw => Fetch, Decode, MemAddr, MemRead, MemWriteback (states 0,1,2,3,4)

Sw => Fetch, Decode, MemAddr, MemWrite (states 0,1,2,5)




Expected:

add => Fetch, Decode, RtypeEx, RtypeWb (states 0,1,6,7 & funct 20)

sub => Fetch, Decode, RtypeEx, RtypeWb (states 0,1,6,7,0 & funct 22)

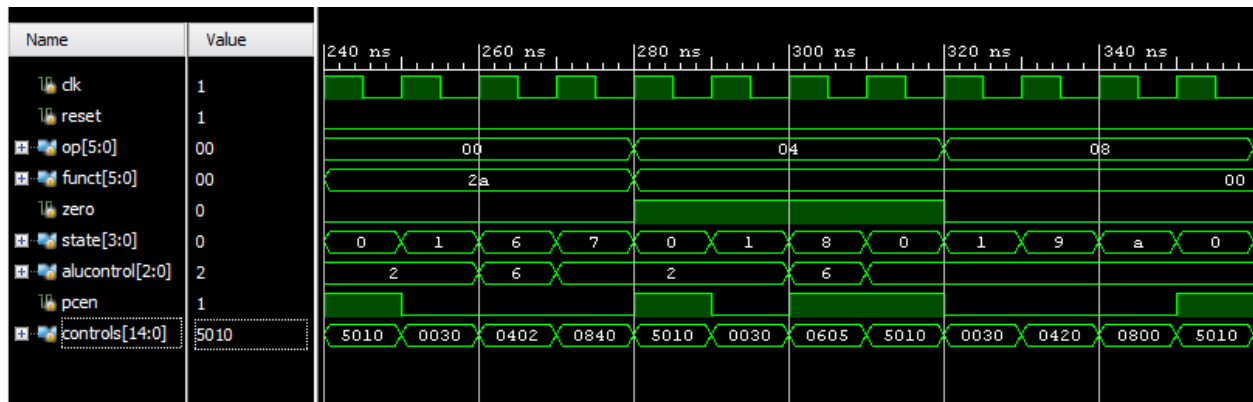or => Fetch, Decode, RtypeEx, RtypeWb (states 0,1,6,7,0 & funct 25)




Expected:

slt => Fetch, Decode, RtypeEx, RtypeWb (states 0,1,6,7)

beq => Fetch, Decode, Branch (states 0,1,8)

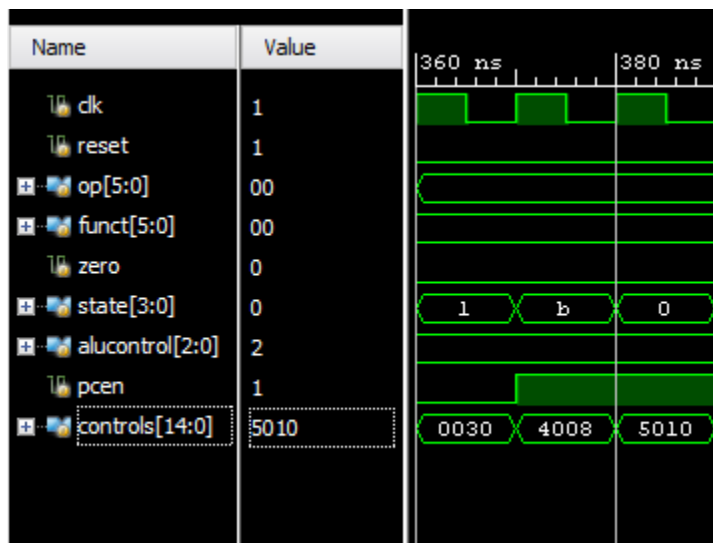addi => Fetch, Decode, AddiEx, AddiWb (states 0,1,9,a)



Expected:

j => Fetch, Decode, Jump (states 0,1,b)

Yes, all the simulation matches the expected values outlined in the captions, which correspond to the table 4 and processor state diagram.